

### Zadatak 1


U kolu na slici 1, poznatih parametara  $C$  i  $R = r = \sqrt{\frac{L}{C}}$ ,

deluje strujni generator  $i_g(t) = I(h(t) - h(t-T))$ ,  $T = RC$ .

Rešavanjem kola u vremenskom domenu odrediti:

[70] a) Indicionu funkciju za struju  $i_1(t)$ .

[30] b) Struju  $i_L(t)$ , za  $t \geq 0$ .

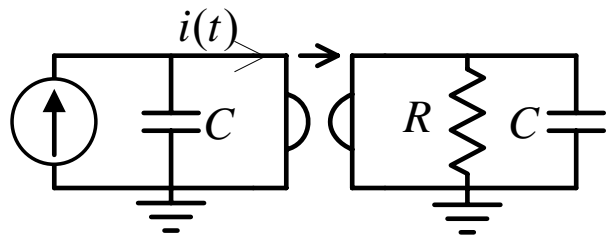

Slika 1


**1 Zadatak** Slika 1 a

$$(D^2 + 2\alpha D + 4\alpha^2)i_L = 4\alpha^2 \cdot i_g; \quad \alpha = \frac{1}{2RC}$$

a)

$$f(t) = \{1 - e^{-\alpha t} [\cos(\sqrt{3}\alpha t) + \frac{1}{\sqrt{3}} \sin(\sqrt{3}\alpha t)]\} h(t)$$

b)  $i_L(t) = I \cdot f(t) - I \cdot f(t-T)$

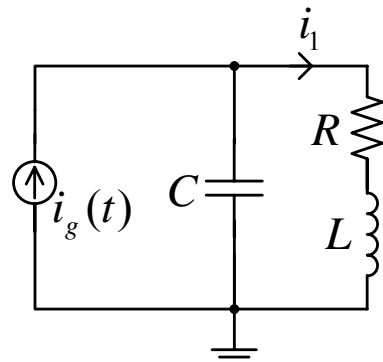

Slika 1a

### Zadatak 2


Parametri  $L, C$  i  $R = r = \sqrt{\frac{L}{C}}$ , kola sa slike 2, su poznati.

Odrediti:

[40] a) Ulaznu admitansu mreže vezane za krajeve generatora ,  $\underline{Y}_{ul}(s) = I / \underline{U}_g$ .

[40] b) Trenutnu vrednost struje generatora  $i(t)$  za  $u_g(t) = 5U \cos \omega_1 t + 13U \cos 2\omega_1 t + U \cos 3\omega_1 t$ , pri čemu je  $\omega_1 = 1/(3\sqrt{LC})$ .

[20] c) Efektivne vrednosti napona i struje generatora.

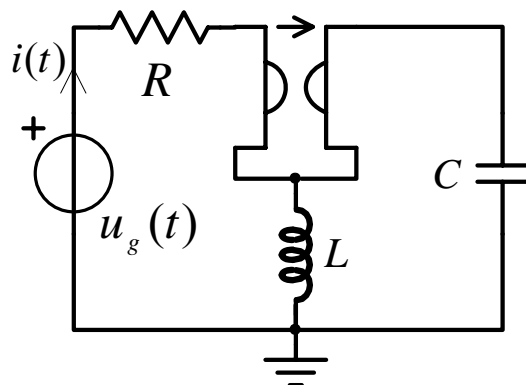

Slika 2.

2.a)  $\underline{Y}_{ul} = \frac{1 + s^2 R^2 C^2}{R(s^2 R^2 C^2 + 2sRC + 1)}$ ;

b)  $\underline{Y}_{ul}^{(n)} = \frac{\omega_0^2 - n^2 \omega_1^2}{R(\omega_0 + jn\omega_1)^2}$ ,  $\omega_0 = \frac{1}{RC} = 3\omega_1$

$\underline{I}^{(n)} = \underline{Y}_{ul}^{(n)} \cdot \underline{U}_g^{(n)}$ ,

$\underline{I}^{(1)} = \frac{4U}{\sqrt{2}R} e^{-j \arg(\frac{3}{4})} \rightarrow i^{(1)}(t) = \frac{4U}{R} \cos(\omega_1 t - \arctg \frac{3}{4})$

$\underline{I}^{(2)} = \frac{5U}{\sqrt{2}R} e^{-j \arg(\frac{12}{5})} \rightarrow i^{(2)}(t) = \frac{5U}{R} \cos(2\omega_1 t - \arg \frac{12}{5})$

$\underline{I}^{(3)} = 0 \rightarrow i^{(3)}(t) = 0$  pa je

$i(t) = \frac{4U}{R} \cos(\omega_1 t - \arg \frac{3}{4}) + \frac{5U}{R} \cos(2\omega_1 t - \arg \frac{12}{5})$

c)  $U_{eff} = U \sqrt{\frac{195}{2}}$ ,  $I = \frac{U}{R} \sqrt{\frac{41}{2}}$ .

### Zadatak 1


U kolu poznatih parametara (slika 1)  $R, L$  i  $C = \frac{4L}{5R^2}$ , deluje strujni

generator  $i_g(t) = \frac{I \cdot t}{RC} h(t)$ . Struja kalema u trenutku  $t = 0$  iznosi

$i_L(0^-) = I_0$ . Odrediti:

a)[30] diferencijalnu jednačinu odziva napona kondenzatora  $u_C(t)$ ,

b)[50] i rešavanjem kola u vremenskom domenu, napon kondenzatora  $u_C(t)$  za  $t \geq 0$ .

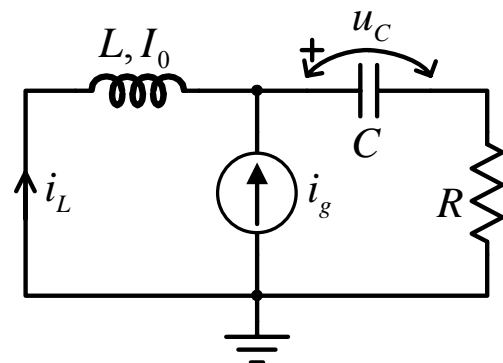

Slika 1

$$a) (D^2 + 2\alpha D + \frac{1}{LC}) \cdot u_c = \frac{1}{C} \cdot D i_g; \quad \alpha = \frac{R}{2L}$$

$$b) (D^2 + 2\alpha D + \frac{1}{LC}) \cdot u_c = \frac{I}{RC^2}, \quad t \geq 0.$$

$$\underline{s}_{1,2} = -\alpha \pm j\omega_1, \quad \omega_1 = 2\alpha,$$

$$u_c(t) = (A \cdot \cos \omega_1 t + B \cdot \sin \omega_1 t) \cdot e^{-\alpha t} + u_{cp}(t)$$

$$u_{cp}(t) = \text{const} = \frac{5}{4} RI, \quad i_g(0^-) = 0,$$

$$Du_c(0^-) = \frac{i_c(0^-)}{C} = \frac{1}{C} [i_L(0^-) + i_g(0^-)] = \frac{I_0}{C},$$

$$Du_c(0^-) = -\alpha A + 2\alpha B = \frac{I_0}{C}$$

$$A = -\frac{5}{4} RI, \quad B = \frac{5}{4} R \left( \frac{I}{2} - I_0 \right),$$

$$u_c(t) = \frac{5}{4} RI \left\{ 1 - \left[ \cos \omega_1 t + \left( \frac{1}{2} - \frac{I_0}{I} \right) \cdot \sin \omega_1 t \right] \cdot e^{-\alpha t} \right\} \cdot h(t).$$

### Zadatak 3

[20+40+40] U kolu poznatih parametara (slika 3)  $R, L$  i


$C = \frac{L}{5R^2}$ , deluje generator konstantne struje  $i_g(t) = I$ .

Prekidač se nalazi u položaju (1) i kolo je u ustaljenom režimu.

U trenutku  $t = t_0$  prekidač se prebaci u položaj (2). Primenom

Laplace-ove transformacije odrediti napon kondenzatora

$u_c(t)$  za  $t \geq 0$ .

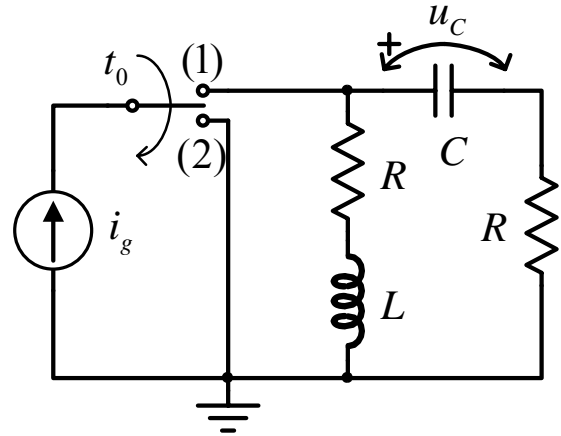

Slika 3

Za  $0 \leq t < t_0$  Slika 3a Samo ispit

$$\begin{aligned} \underline{U}_c &= \frac{\frac{s}{C} - \frac{\alpha}{C}}{s^2 + 2\alpha s + \omega_0^2} I_g = \frac{1}{C} \frac{s - \alpha}{(s + \alpha)^2 + \omega_1^2} \cdot \frac{I}{s} = \\ &= \frac{I}{\omega_1 C} \frac{\omega_1}{(s + \alpha)^2 + \omega_1^2} + \frac{1}{C} \frac{\alpha}{(s + \alpha)^2 + \omega_1^2} \cdot \frac{I}{s} = \\ &= I \frac{1}{\omega_1 C} \frac{\omega_1}{(s + \alpha)^2 + \omega_1^2} + \frac{RI}{s} - RI \frac{s + \alpha}{(s + \alpha)^2 + \omega_1^2} - \frac{RI}{2} \frac{\omega_1}{(s + \alpha)^2 + \omega_1^2} \\ &\xrightarrow{L-1} u_c(t) = RI \left\{ 1 + e^{-\alpha t} [2 \sin(\omega_1 t) - \cos(\omega_1 t)] \right\} 0 < t < t_0 \end{aligned}$$

Ispit i kolokvijum:


Za  $t = t_0$ ,  $i_L(t_0^-) = I = -I_0$ ,  $u_c(t_0^-) = RI = U_0$ .

Za  $t \geq t_0$ ,  $\tau = t - t_0$ . Slika 3b


$$\begin{cases} 2RI + Ls\underline{I} - LI_0 + \underline{U}_c = 0, \\ \underline{I} = C s \underline{U}_c - C U_0 \end{cases} \Rightarrow \underline{I} = \frac{s I_0 - \frac{U_0}{L}}{s^2 + 2 \frac{R}{L} s + \frac{1}{LC}}$$

$$\left\{ \begin{aligned} \underline{I} &= I_0 \frac{s + \alpha}{(s + \alpha)^2 + \omega_1^2} - \underbrace{\frac{I_0}{2} \frac{\omega_1}{(s + \alpha)^2 + \omega_1^2} - \frac{U_0}{\omega_1 L} \frac{\omega_1}{(s + \alpha)^2 + \omega_1^2}}_{=0}; \\ \alpha &= \frac{R}{L}, \quad \omega_1 = 2\alpha, \quad -\frac{I_0}{2} = \frac{U_0}{\omega_1 L} = \frac{RI}{\frac{R}{L} 2L} = \frac{I}{2}. \end{aligned} \right\}$$

$$\xrightarrow{\mathcal{L}^{-1}} i(t) = -I \cdot e^{-\alpha(t-t_0)} \cdot \cos[\omega_1(t-t_0)] \cdot h(t-t_0)$$

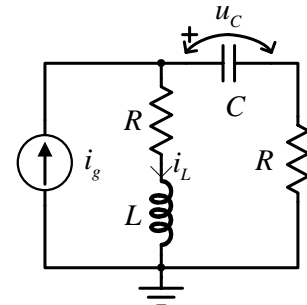

Slika 3a

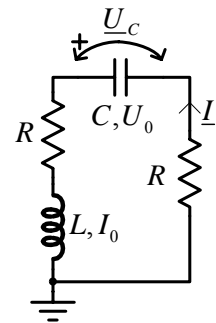

Slika 3b